
### Assignment

Name – Sreekar Addanki


Reg No - 20BCY10127

Campus – Bhopal


# 1 Led traffic light

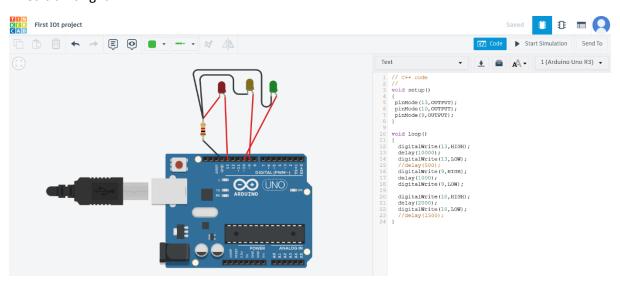


# 2 Digital Read

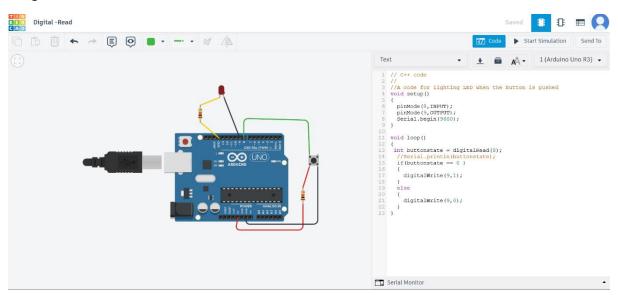


### 3 Potentiometer Circuit

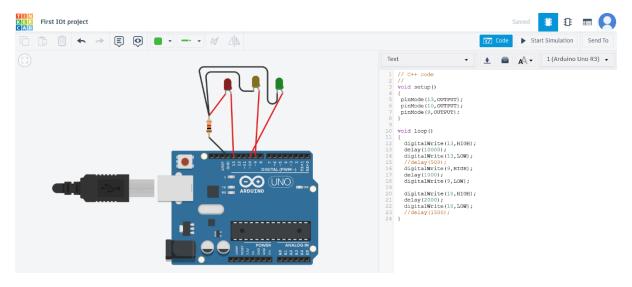


## 4 Grand Bigery-Snicket

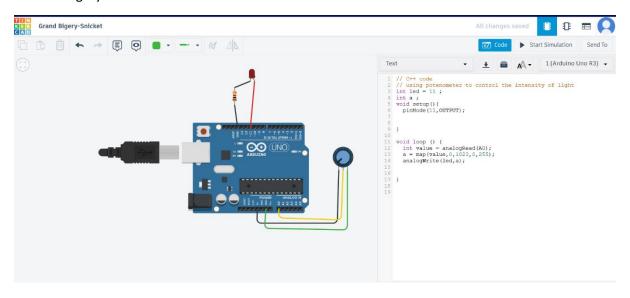


### 5 Ultrasound distance sensor

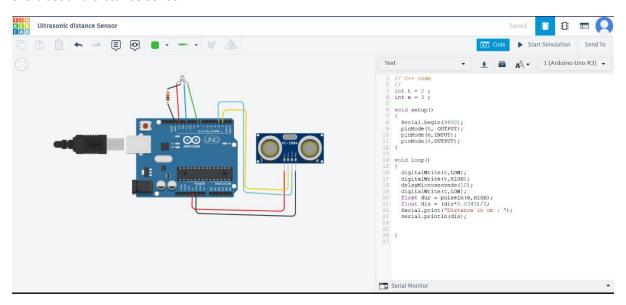

### Temperature sensor

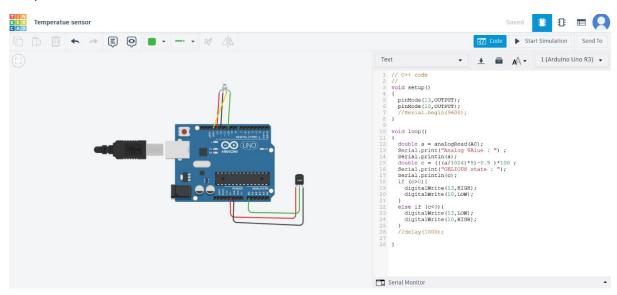

### PIR senor

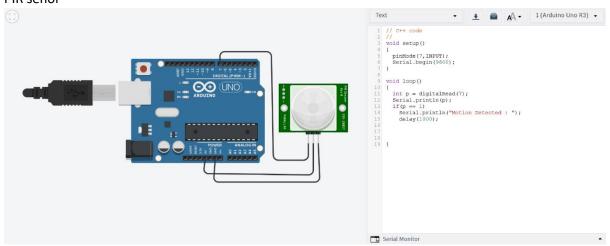

### Servo Motors

